

# Analysis of Flip Flop Circuits

---

# Analysis of Sequential Logic Circuits

---

- \* State equations are similar to Boolean expressions from combinational logic
  - Describe the output and transition logic of circuit
- \* State table is similar to a truth table
  - Describes state transition and output given combination of inputs
- \* State diagrams are visual representations of the state table

# Circuit to State Equation

- \* State equation is the Boolean expression for circuit


- \* Will have multiple equations

- One for output of circuit ( $F$ )

- One to describe, state, or input to flip flops

- \* Each flip flop is designated A,B,C,...etc.



- \* Input and output to flip flop is A

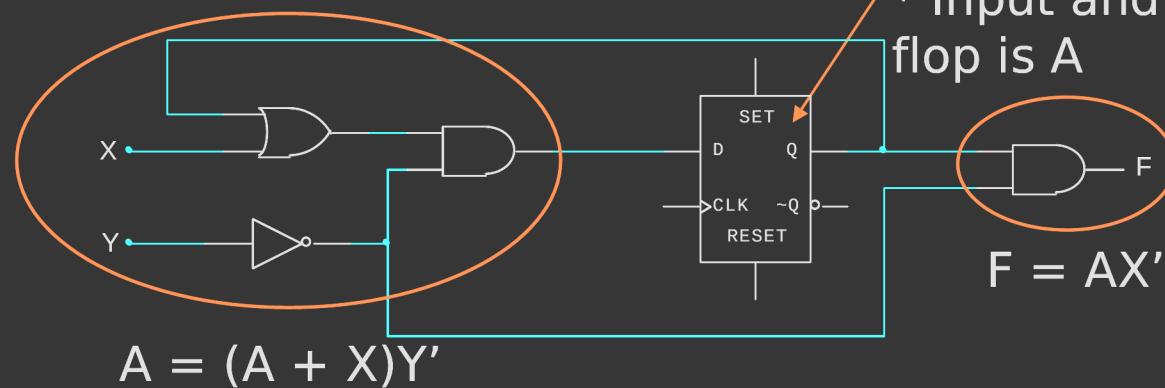
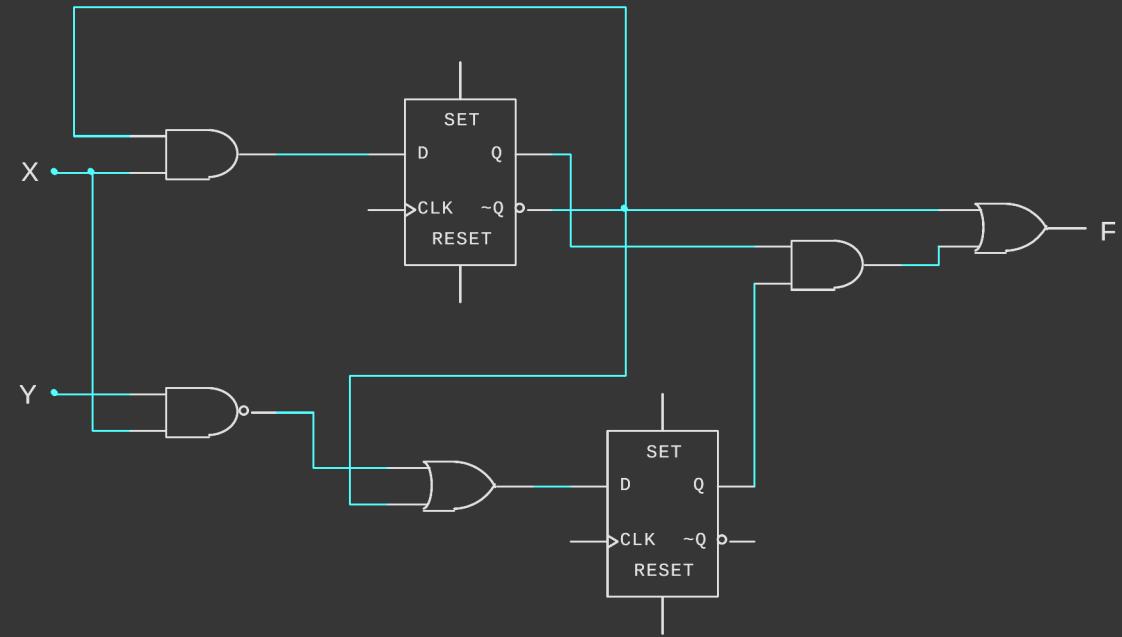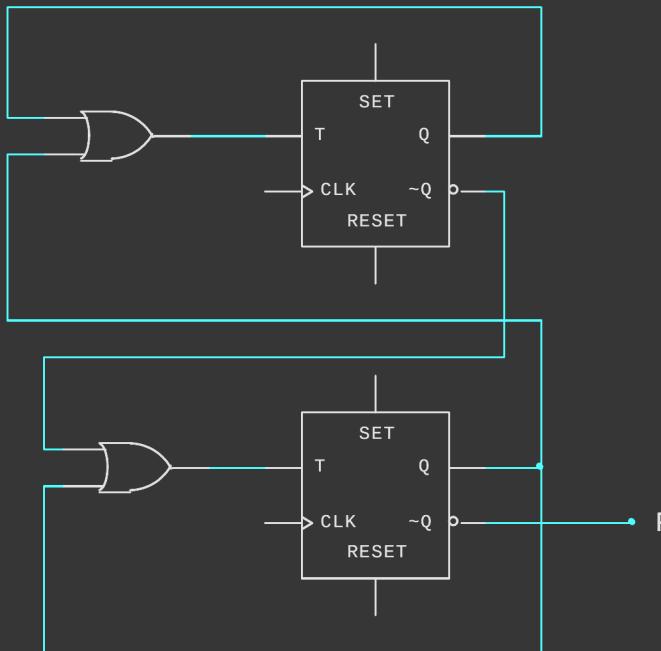
# Example

---

What are the state equations for following circuits?



# State Table

\* Similar to a truth table, it describes all the possible outputs given input combinations

- Inputs include current output of flip flops (A,B,..etc.) and input of circuit (X,Y,..etc.)
- Outputs include next output of flip flops (A,B,..etc.) and output of circuit (F,G,..etc.)


Present State		Input	Next State		Output
A	B	x	A	B	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1

Flip Flops current output      Input to circuit      Flip Flops next output      Output of circuit

Input to state table      Output of state table
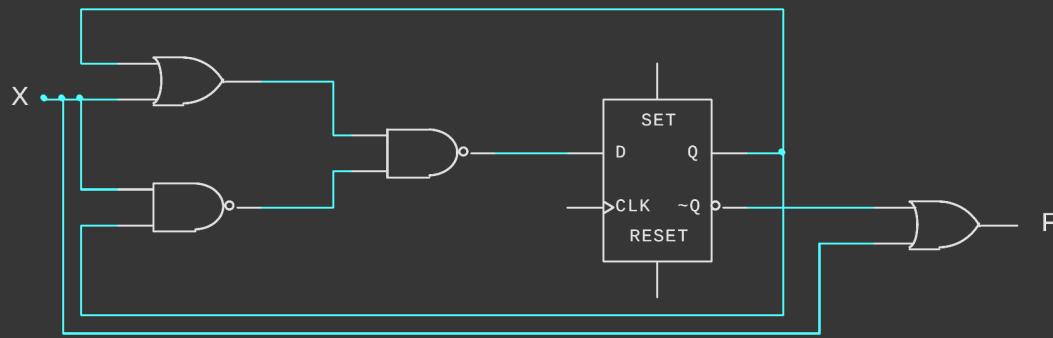
# Example

Create a State Table for the following circuit



Present State	Input	Next State	Output
A	X	A	F
0	0		
0	1		
1	0		
1	1		

# State Table to K-map

\* Each column of a state table output can be simplified with a K - map

Present State		Input	Next State		Output
A	B	x	A	B	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1

3 K – maps in total

# Example

---

Use K – Map to draw the logic circuit from the state table

Present State		Input	Next State		Output
A	B	x	A	B	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1


# Example

# Finite State Machine

\* Diagram showing all states, how to transition from state to state, and output at each state


\* **Mealy** – Output depends on current state and input. Output changes immediately

\* **Moore**  
clocking  $\epsilon$

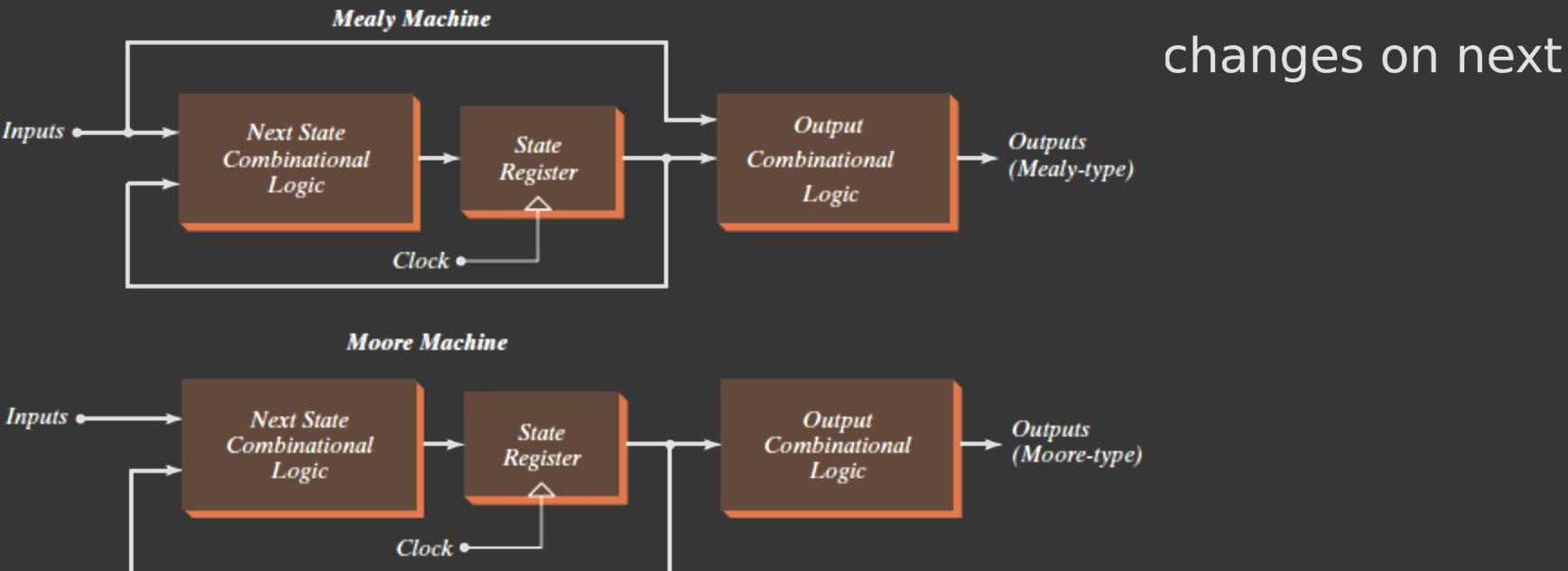

# Mealy State Diagram


---

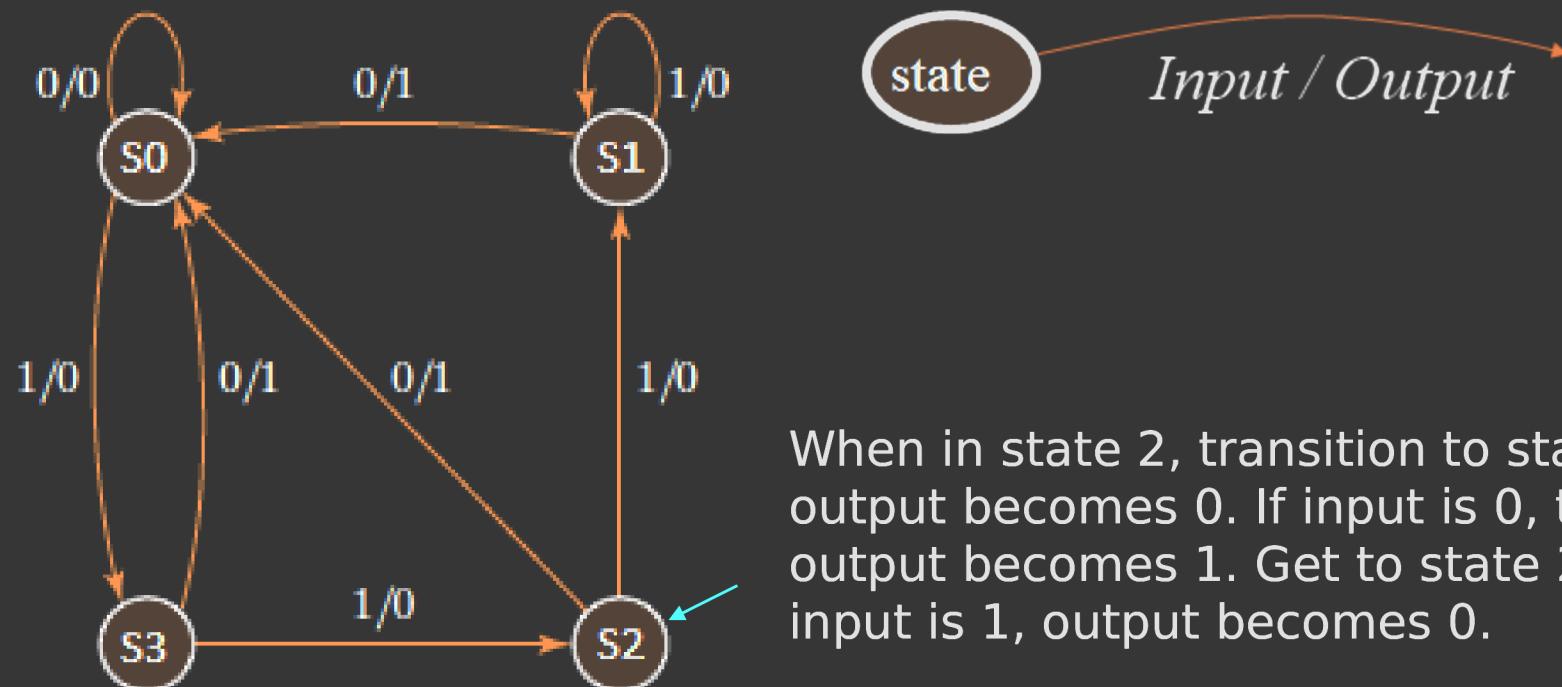

When in state 2, transition to state 1 if input is 1, output becomes 0. If input is 0, transition to state 0, output becomes 1. Get to state 2 from state 3 if input is 1, output becomes 0.

# Moore State Diagram


---

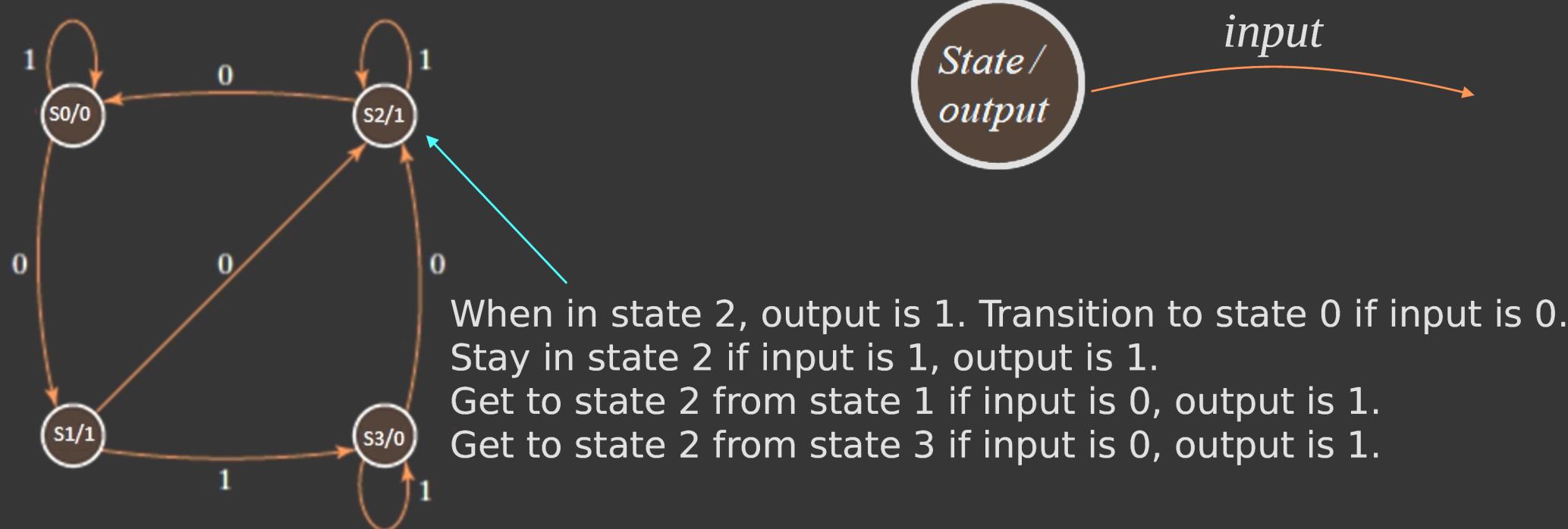
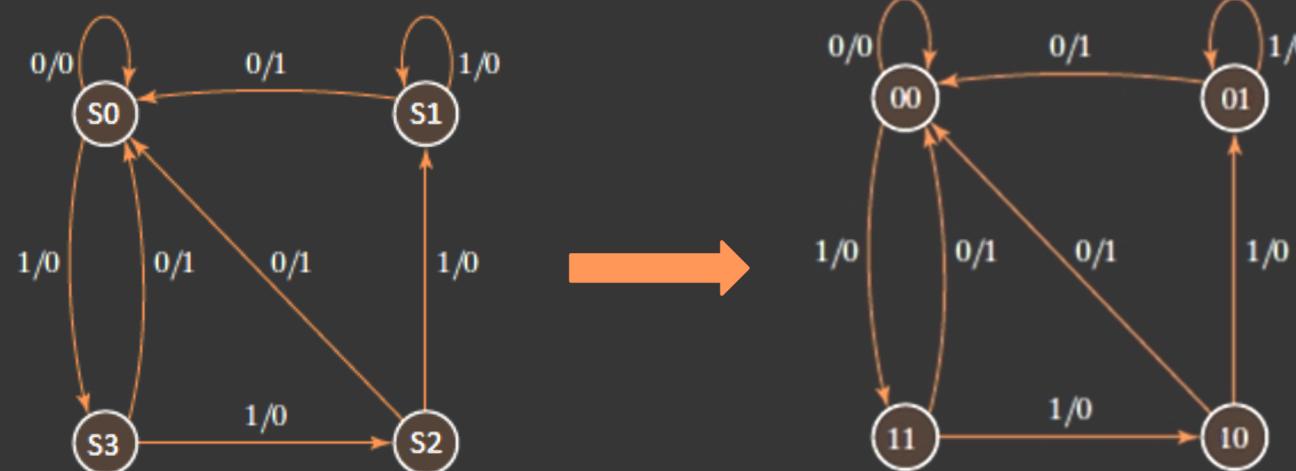
# Encode States


- \* States are encoded as binary values to design FSM into a logic circuit
- \* Make each state a binary number
- \* Previous examples had 4 states, so 2 bits are used to represent each state.  
Each bit is 1 flip flop

- $S_0 \rightarrow 00$
- $S_1 \rightarrow 01$
- $S_2 \rightarrow 10$
- $S_3 \rightarrow 11$


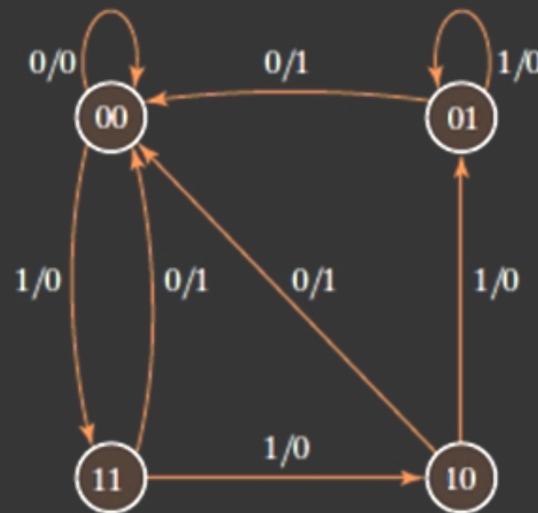
# Creating State Table


\* Use encoded state values and input to create table for next state and output. A and B are a single bit from state encoding.



	Present State		Input <i>x</i>	Next State		Output <i>y</i>
	A	B		A	B	
S0	0	0	0	0	0	0
S1	0	0	1	1	1	0
S2	0	1	0	0	0	1
S3	0	1	1	0	1	0
	1	0	0	0	0	1
	1	0	1	0	1	0
	1	1	0	0	0	1
	1	1	1	1	0	0

Mealy FSM

# Moore State Table

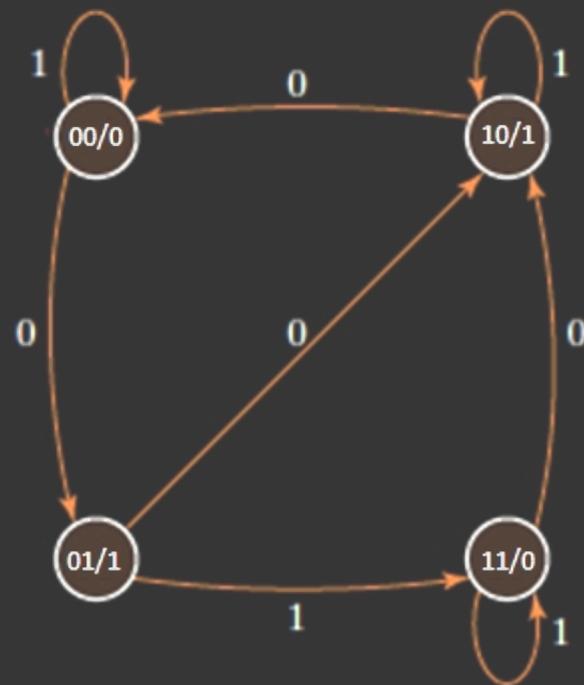

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	1	0

Output is dependent  
on present state

# K - Map State Table

---


Inputs on K-Map

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	0	0	0	1
1	1	1	1	0	0

K-Map outputs (each column will need a K-Map)


# K - Map

Present state and input from state table

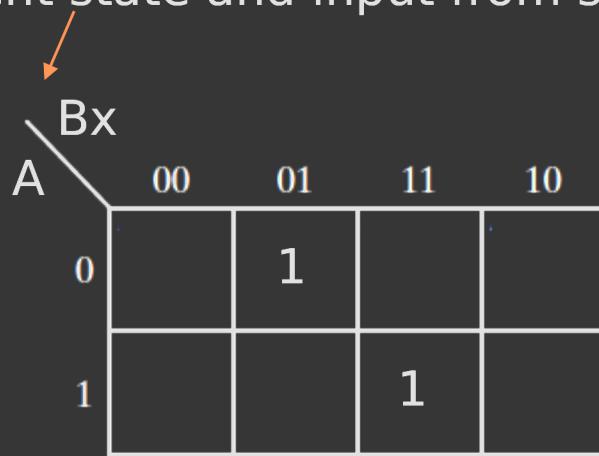


A K-map showing the present state of a system. The columns are labeled A (top-left) and Bx (top-right). The rows are labeled 0 (left) and 1 (right). The cells are labeled as follows:

	00	01	11	10
0		1		
1			1	

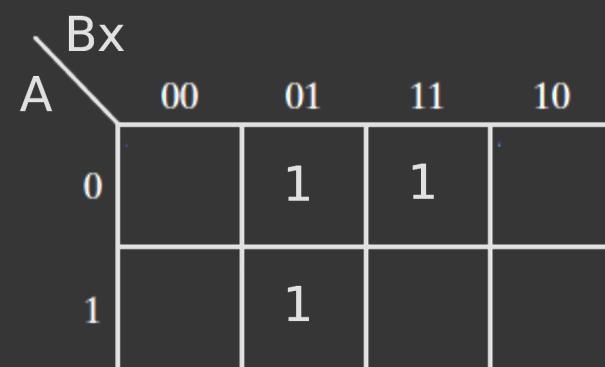


A K-map showing the next state of the system. The columns are labeled A (top-left) and Bx (top-right). The rows are labeled 0 (left) and 1 (right). The cells are labeled as follows:

	00	01	11	10
0		1	1	
1		1		

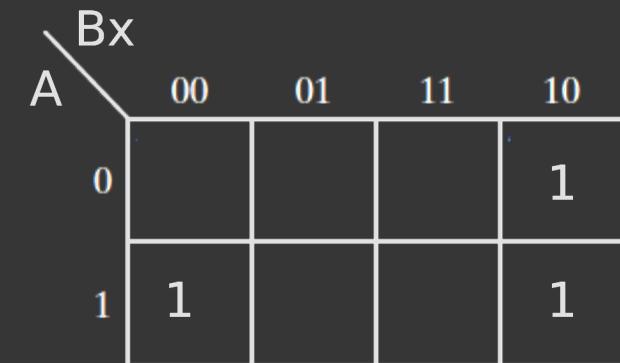

A K-map showing the output of the system. The columns are labeled A (top-left) and Bx (top-right). The rows are labeled 0 (left) and 1 (right). The cells are labeled as follows:


	00	01	11	10
0				1
1	1			1

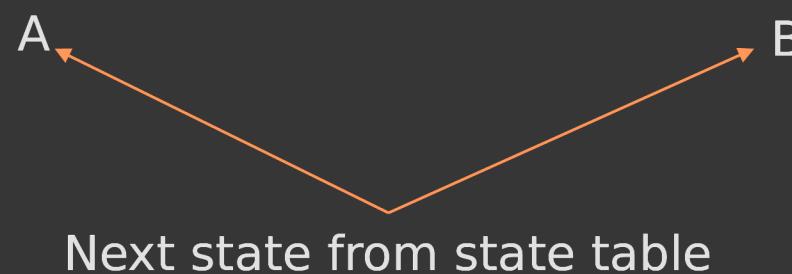


output from state table

# K - Map


---

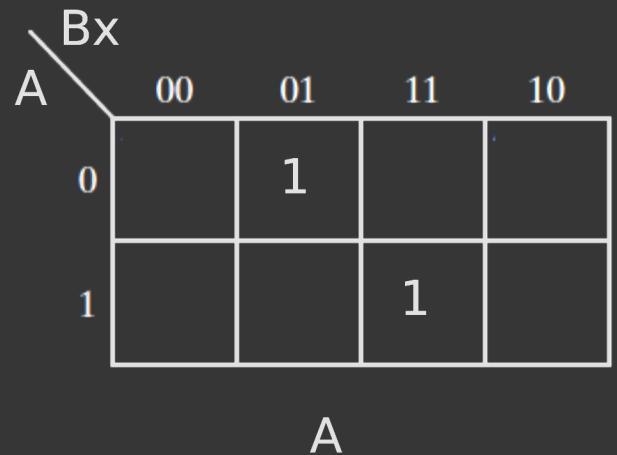

$$A = A'B'x + ABx$$

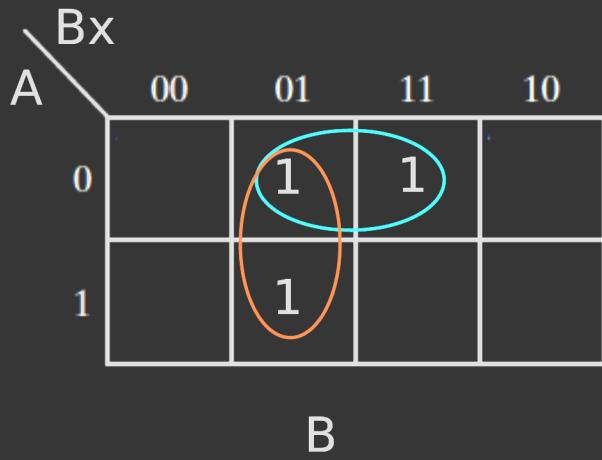


$$B = B'x + A'x$$

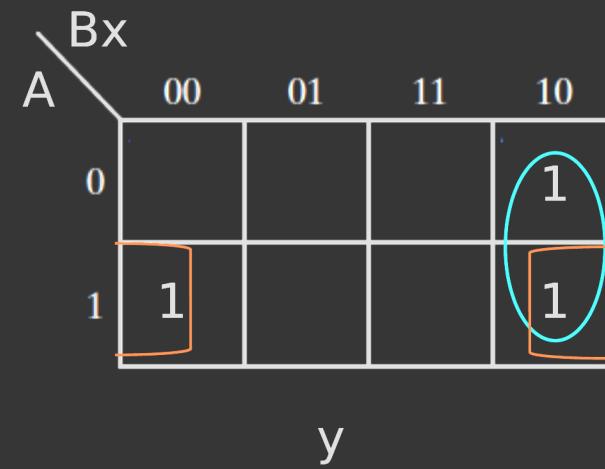

$$y = Bx' + Ax'$$
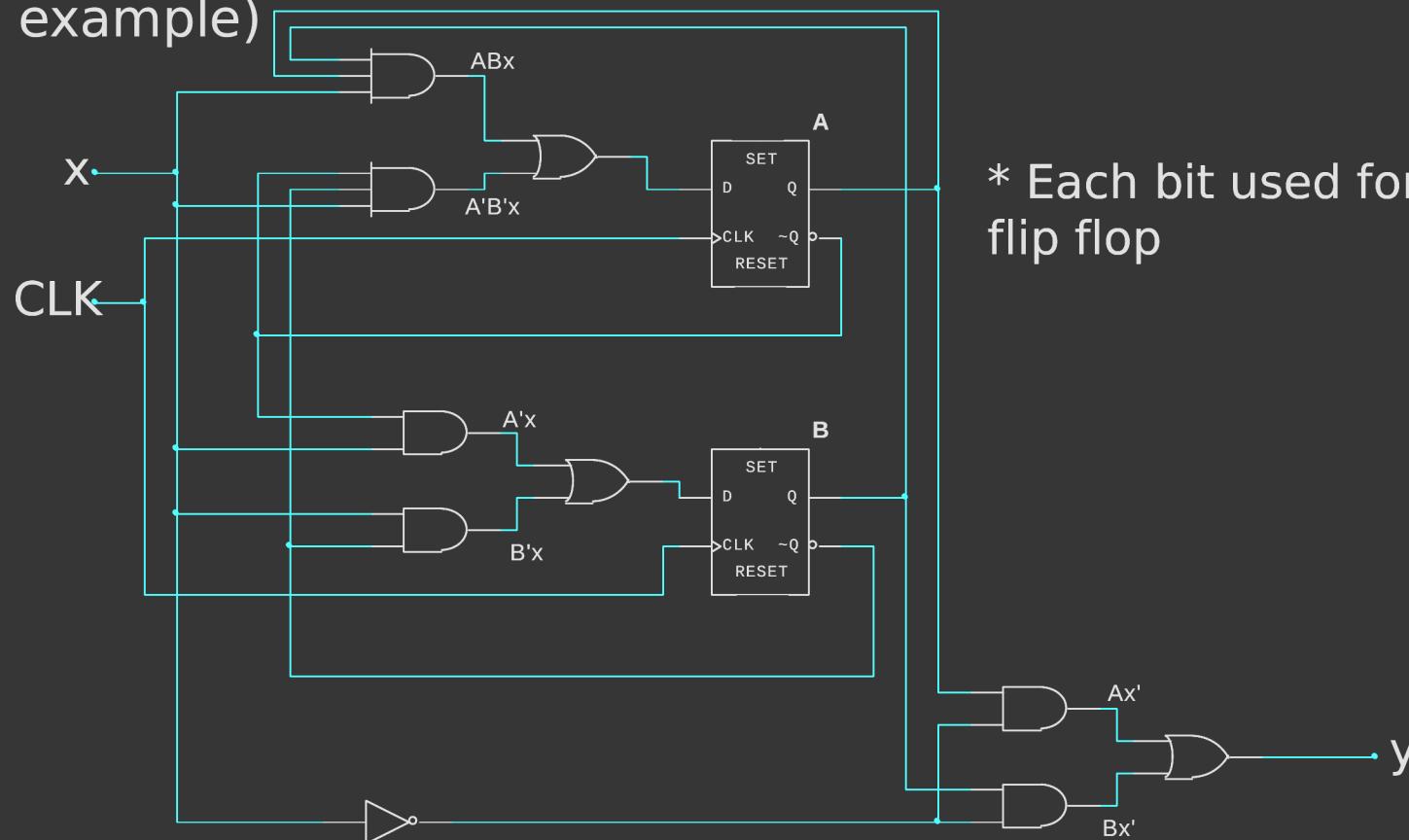
# Build Logic Circuit

\* A and B are flip flop output and fed back into flip flop input. (Using D Flip Flop in example)



\* Each bit used for state encoding is a flip flop

# What if State Doesn't Exist?

---

- \* Mark states that don't exist as “don't care”, or X on a state table
- \* Same applies if a transition does not exist as well
- \* Use the X when creating k-map to try and simplify circuit

# Example

---

\* Given the following state diagram create the state table and logic circuit

