


Analysis of Flip Flop Circuits

Analysis of Sequential Logic Circuits

- * State equations are similar to Boolean expressions from combinational logic
 - Describe the output and transition logic of circuit
- * State table is similar to a truth table
 - Describes state transition and output given combination of inputs
- * State diagrams are visual representations of the state table



Circuit to State Equation

 - * State equation is the Boolean expression for circuit
- * Will have multiple equations
 - One for output of circuit (F)
 - One to describe, state, or input to flip flops
- * Each flip flop is designated A,B,C,...etc.
- * Input and output to flip flop is A



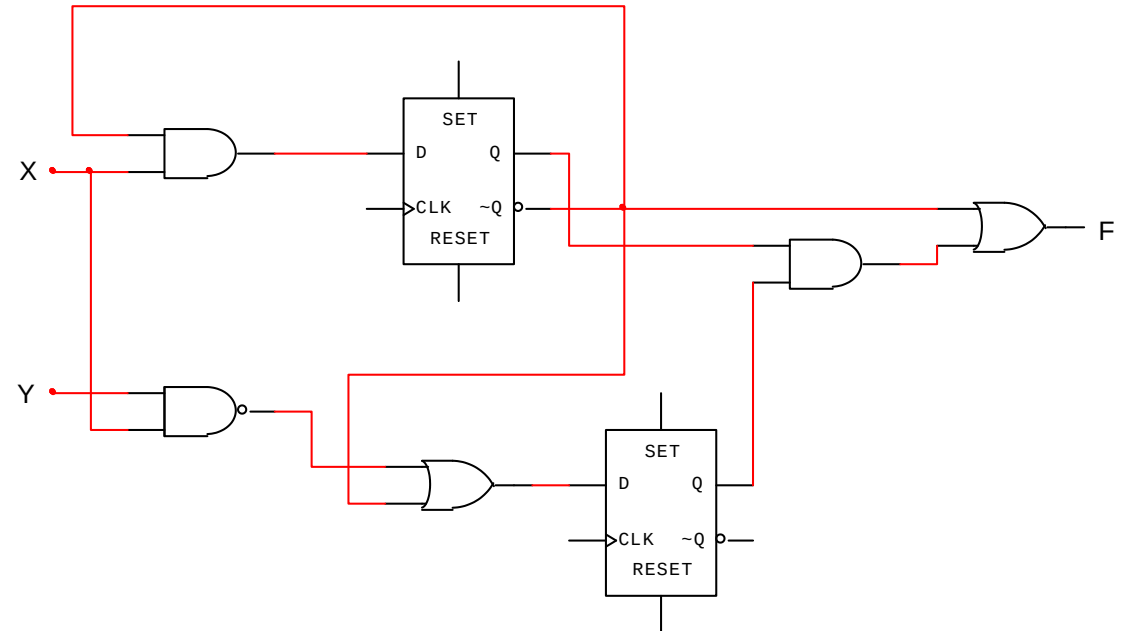 Example

What are the state equations for following circuits?



State Table

* Similar to a truth table, it describes all the possible outputs given input combinations

- Inputs include current output of flip flops (A,B,..etc.) and input of circuit (X,Y,..etc.)
- Outputs include next output of flip flops (A,B,..etc.) and output of circuit (F,G,..etc.)

Input to circuit

Flip Flops next output

Flip Flops current output

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1


Output of circuit

 Input to state table

 Output of state table

 Example

Create a State Table for the following circuit



Present State	Input	Next State	Output
A	X	A	F
0	0		
0	1		
1	0		
1	1		

State Table to K-map

* Each column of a state table output can be simplified with a K - map

Present State		Input	Next State		Output
A	B	x	A	B	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1





3 K - maps in total

Example

Use K – Map to draw the logic circuit from the state table

Present State		Input	Next State		Output
A	B	x	A	B	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	1	1

Example

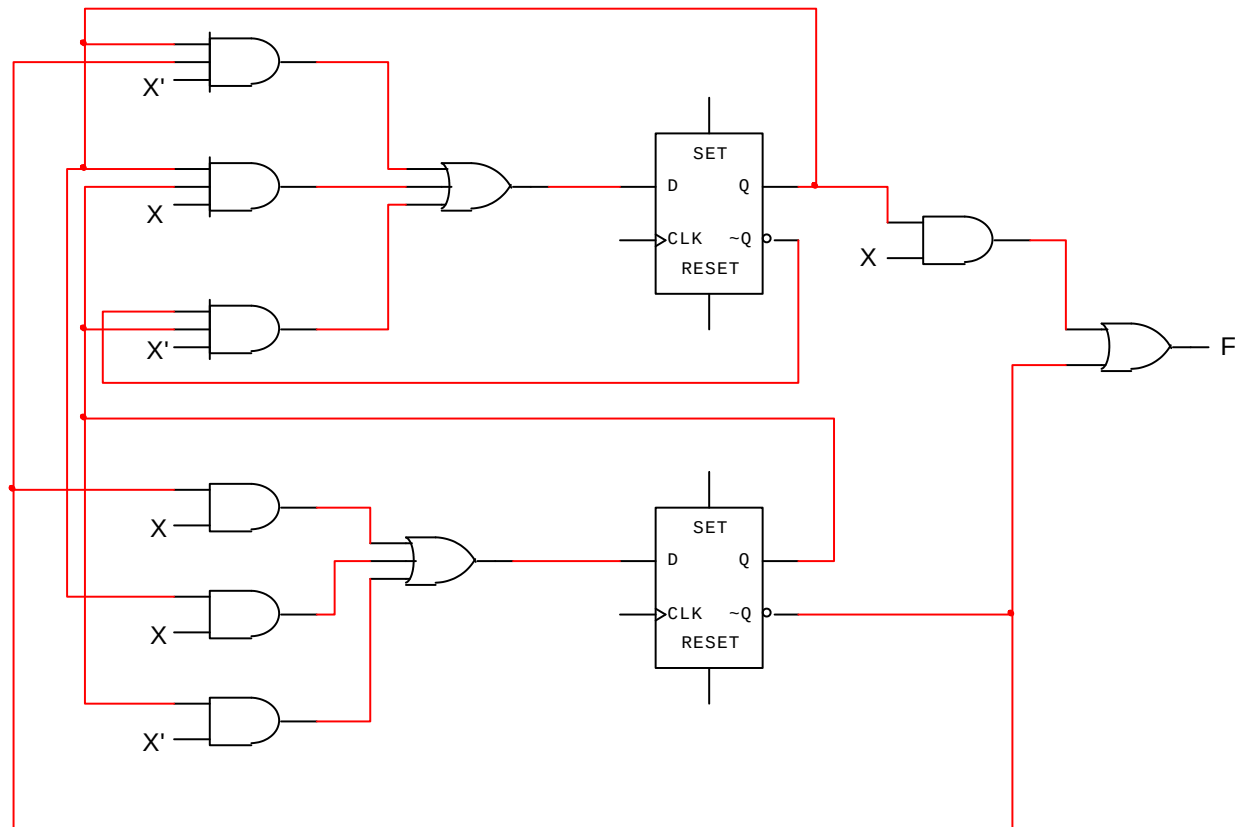 


Finite State Machine

- * Diagram showing all states, how to transition from state to state, and output at each state



- * **Mealy** – Output depends on current state and input. Output changes immediately

- * **Moore**
clocking €

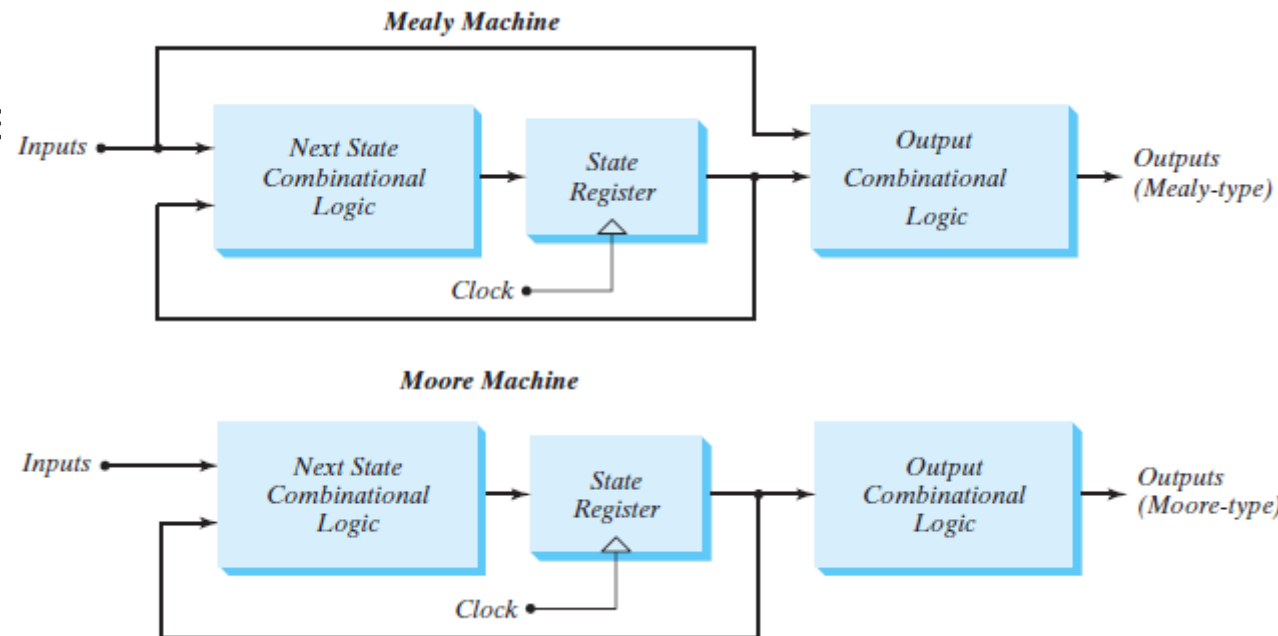



changes on next

Mealy State Diagram

  

When in state 2, transition to state 1 if input is 1, output becomes 0. If input is 0, transition to state 0, output becomes 1. Get to state 2 from state 3 if input is 1, output becomes 0.


Moore State Diagram

  

When in state 2, output is 1. Transition to state 0 if input is 0.
Stay in state 2 if input is 1, output is 1.
Get to state 2 from state 1 if input is 0, output is 1.
Get to state 2 from state 3 if input is 0, output is 1.


Encode States

 - * States are encoded as binary values to design FSM into a logic circuit
- * Make each state a binary number
- * Previous examples had 4 states, so 2 bits are used to represent each state. Each bit is 1 flip flop
 - S0 -> 00
 - S1 -> 01
 - S2 -> 10
 - S3 -> 11



Creating State Table

 * Use encoded state values and input to create table for next state and output. A and B are a single bit from state encoding.



S0

S1


S2

S3

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	0	0	0	1
1	1	1	1	0	0

Mealy FSM

Moore State Table

 

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	1	0

Output is dependent
on present state

K – Map State Table


Inputs on K-Map

Present State			Input	Next State		Output
A	B	x		A	B	y
0	0	0		0	0	0
0	0	1		1	1	0
0	1	0		0	0	1
0	1	1		0	1	0
1	0	0		0	0	1
1	0	1		0	1	0
1	1	0		0	0	1
1	1	1		1	0	0


K-Map outputs (each column will need a K-Map)

K - Map

Present state and input from state table

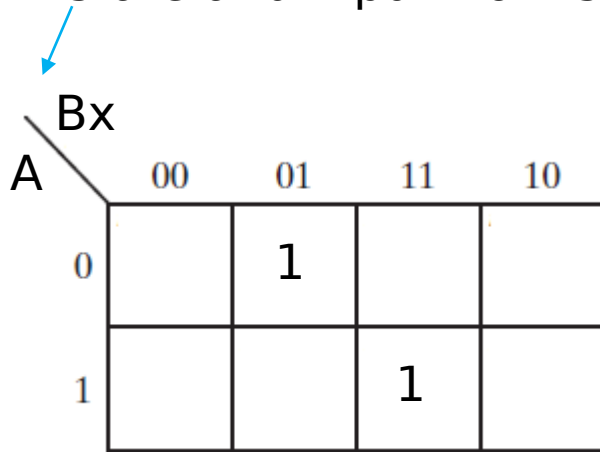


A \ Bx	00	01	11	10
0		1		
1			1	

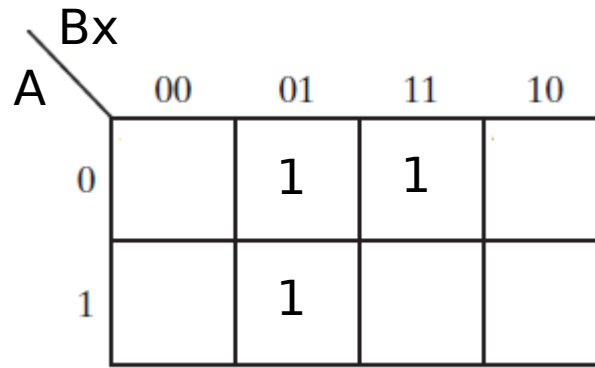

A \ B	00	01	11	10
0		1	1	
1		1		

A B

Next state from state table

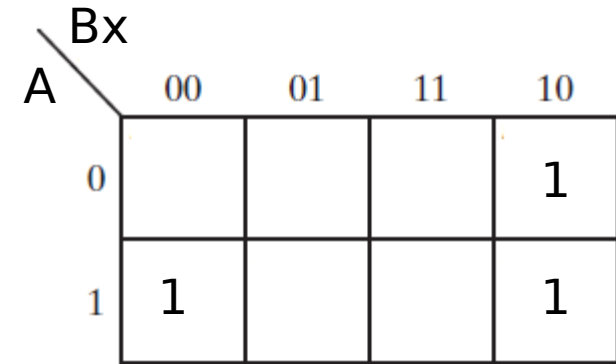

A \ Bx	00	01	11	10
0				1
1	1			1

y

output from state table

K - Map

		Bx			
		00	01	11	10
A	0		1		
	1			1	

A

$$A = A'B'x + ABx$$

		Bx			
		00	01	11	10
A	0		1	1	
	1		1		

B

$$B = B'x + A'x$$


		Bx			
		00	01	11	10
A	0				1
	1	1			1

y

$$y = Bx' + Ax'$$

Build Logic Circuit

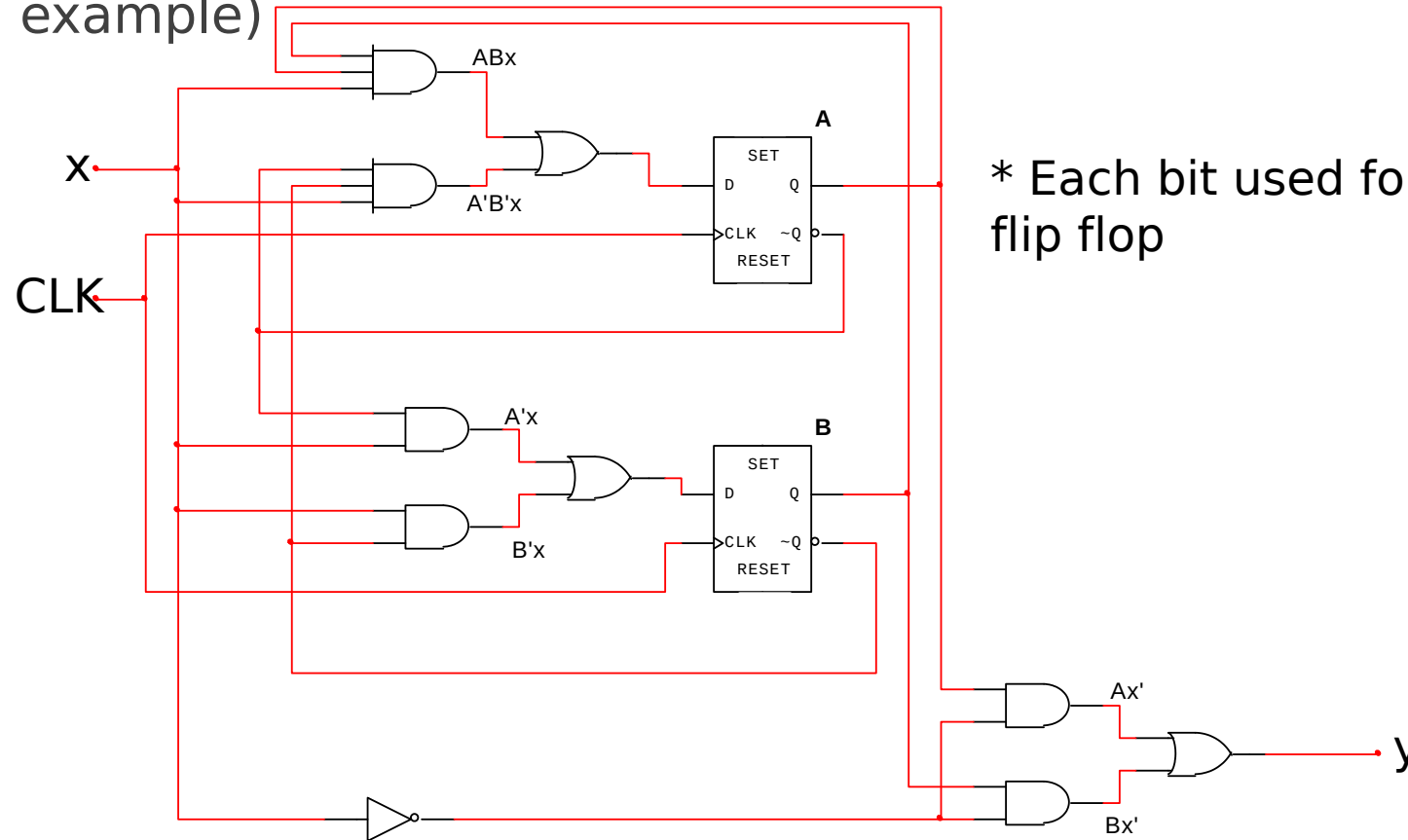* A and B are flip flop output and fed back into flip flop input. (Using D Flip Flop in example)



* Each bit used for state encoding is a flip flop

What if State Doesn't Exist?

- * Mark states that don't exist as “don't care”, or X on a state table
- * Same applies if a transition does not exist as well
- * Use the X when creating k-map to try and simplify circuit

Example

* Given the following state diagram create the state table and logic circuit

